


$$\Rightarrow [\bar{A} + \bar{A} \cdot \bar{B}] \cdot [B + \bar{B} \cdot \bar{C}]$$

$$\Rightarrow [\bar{A} \cdot (\bar{B} + 1)] \cdot [\bar{B} \cdot (\bar{C} + 1)]$$

$$\Rightarrow \bar{A} \cdot \bar{B}$$

$$\Rightarrow \overline{A+B}$$

NOR gate.

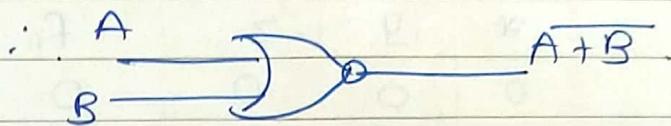

### \* Minterms & Max terms :-

- ① Binary variable can take value of zero or 1.
  - ② A boolean function is an expression formed with binary variables two binary operators (OR and AND), unary operator NOT, parenthesis and equal sign.  
for given value of variable function can be either zero or 1.
- eg.  $f_1 = \bar{x}yz'$   
 $f_2 = (\bar{x}yz' + yz')$

	minterms	maxterms
	term	designation
0 0 0	$\bar{x}'y'z'$	$\bar{x}+y+z$
0 0 1	$\bar{x}'y'z'$	$\bar{x}+y+z'$
0 1 0	$\bar{x}'y'z'$	$\bar{x}+y'+z$
0 1 1	$\bar{x}'y'z'$	$\bar{x}+y'+z'$
1 0 0	$\bar{x}y'z'$	$\bar{x}'+y+z$
0 1 0	$\bar{x}y'z'$	$\bar{x}'+y+z'$
1 0 0	$\bar{x}y'z'$	$\bar{x}'+y'+z$
1 1 1	$\bar{x}y'z'$	$\bar{x}'+y'+z'$

\* conversion from 1 canonical / standard form to another canonical form. ( $SOP \rightarrow POS$ ) OR ( $POS \rightarrow SOP$ )

Interchange the symbols

[ $\Sigma$  to  $\Pi$  &  $\Pi$  to  $\Sigma$ ] and list those nos missing from the original form.

Eg

$$\textcircled{1} \quad f(x, y, z) = \Pi (0, 2, 4, 3) \\ = \Sigma (1, 3, 6, 7)$$

$$\textcircled{2} \quad f(w, x, y, z) = \Sigma_m (1, 7) \\ = \Pi_m (0, 2, 3, 4, 5, 6, 8, 9, 10, \\ 11, 12, 13, 14, 15, 16)$$

Q. I Express boolean function  $f = A + B'C$  in a sum of minterms.



$$\begin{aligned} A &= A(B+B') \cdot (C+C') \\ &= ABC + A'BC + AB'C + A'B'C \end{aligned}$$

$$\begin{aligned} B'C &= (A+A')(B'C) \\ &= AB'C + A'B'C \end{aligned}$$

$$\Rightarrow A + B'C$$

$$\Rightarrow ABC + A'BC + \underline{AB'C} + \underline{AB'C'} + \underline{AB'C} + A'B'C$$

$$\Rightarrow ABC + A'BC + AB'C + AB'C' + A'B'C$$

$$\Rightarrow m_7 + m_6 + m_5 + m_4 + m_1$$

$$= \Sigma_m (7, 6, 5, 4, 1)$$

Q2 Express  $F = \bar{x}y + \bar{x}'z$  in a product of maxterms.

$$\rightarrow F = \bar{x}y + \bar{x}'z$$

first convert function into OR terms using  
xy distributive law.

$$F = \bar{x}y + \bar{x}'z$$

$$= (\bar{x}y + \bar{x}') (\bar{x}y + z)$$

$$= (\bar{x} + \bar{x}') (\bar{x}' + y) (\bar{x} + z) (y + z)$$

$$= 1 (\bar{x}' + y) (\bar{x} + z) (y + z)$$

$$= \bar{x}'$$

$$\bar{x}y + \bar{x}y'z + \bar{x}' + \bar{x}'z$$

$$\bar{x}y + \bar{x}y'z + \bar{x}'z$$

$$\bar{x}y + \bar{x}'z$$

$$z + z'$$

$$\bar{x}' + y = (\bar{x}' + y) + z z'$$

$$= \bar{x}'z z' + (\bar{x}' + y + z) (\bar{x}' + y + z')$$

$$\Rightarrow M_4 \cdot M_5$$

$$\overline{BC}$$

$$\bar{x} + z = (\bar{x} + z) + yy'$$

$$= (\bar{x} + \overset{\circ}{z} + \overset{\circ}{y}) (\bar{x} + \overset{\circ}{z} + \overset{\circ}{y}')$$

$$= M_0 \cdot M_2$$

$$\overline{BC}$$

$$y + z = (y + z) + \cancel{\bar{x}}\bar{x}'$$

$$= (\overset{\circ}{x} + \overset{\circ}{y} + \overset{\circ}{z}) (\overset{\circ}{x}' + \overset{\circ}{y}' + \overset{\circ}{z})$$

$$= M_0 \cdot M_4$$

$$F = (\bar{x}'y) (\bar{x} + z) (y + z) \Rightarrow M_0 M_2 M_4 M_5$$

$$\Rightarrow \odot \prod_M (0, 2, 4, 5)$$

## # Karnaugh Map (K-map)

(Simplification of Boolean function by K-map)

- The map method provides a simple straightforward procedure for minimizing Boolean function. It is diagram made up of square. Each square represent 1 minterms. Since any Boolean function can be expressed as sum of minterms be follows that a Boolean function is recognised graphically in map form area enclosed by those square whose minterms are in Boolean function.
- In fact, the map present a visual diagram of all possible.
- A function may be expressed in std form.
- By recognising various patterns used can derived alternative algebraic expression for the same function, from which he/she can select the simplest function.
- We shall assume that simplest algebraic expression is anyone in a sum of product or product of sum & it has minimum no. of literals.
- This expression is not necessarily unique.

Two

~~minutems~~

0	0	0
0	$x'y'$	$xy$
0	$xy'$	$xy$
1	2	3

~~minutems~~

0	0	0
0	$xy$	$xy$
0	$x'y'$	$xy$
1	2	3

\* Three variable Map :

minterms

		$y'z'$	$y'z$	$yz$	$yz'$
		00	01	11	10
$x'z$	0	$x'y'z'$	$x'y'z$	$xy'z$	$xy'z'$
$x'z$	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$

maxterms


$x$	$y+z$	$y+z'$	$y'+z$	$y'+z'$
0	$0+0$	$0+1$	$1+1$	$1+0$
1	$x+y+z$	$x+y+z'$	$x+y'+z$	$x+y'+z'$
	(1)	(1)	(1)	(1)

$x$	$x+y+z$	$x+y+z'$	$x+y'+z$	$x+y'+z'$
0	$x+y+z$	$x+y+z'$	$x+y'+z$	$x+y'+z'$
1	$x+y'+z$	$x+y'+z'$	$x+y+z$	$x+y+z'$
	(1)	(1)	(1)	(1)

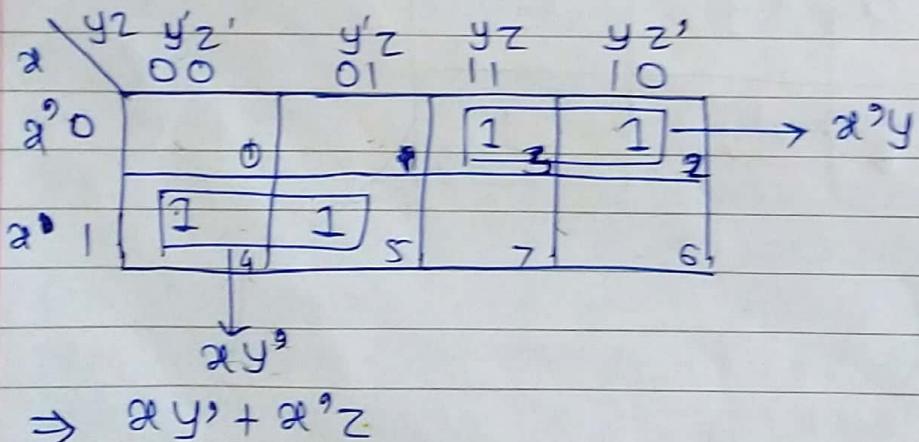
Q.1 Simplify boolean function by K-map.

$$\begin{aligned}
 F &= x'y'z + x'y'z' + xy'z' + xy'z \\
 &= m_3 + m_2 + m_4 + m_5 \\
 &= \Sigma(3, 2, 4, 5).
 \end{aligned}$$



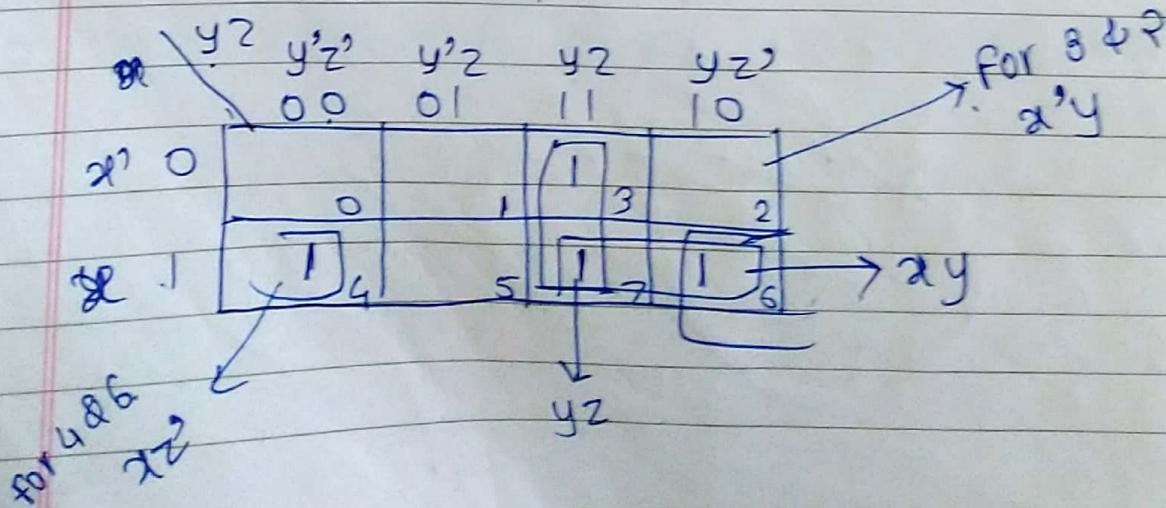Q.2

$$\begin{aligned}
 F &= x'y'z + x'y'z' + xy'z + xyz' \\
 &= m_3 + m_4 +
 \end{aligned}$$



\* Four variable map :

minterms

	$wz'$	$w'z$	$wz$	$w'z'$	0000	0
	00	01	11	10	0001	1
	00	01	11	10	0010	2
$\bar{x}y' 00$	$\bar{x}'y'wz'$	$\bar{x}'y'wz$	$\bar{x}'y'wz$	$\bar{x}'y'wz'$	0011	3
$x'y' 01$	$\bar{x}'y'wz'$	$\bar{x}'y'wz$	$\bar{x}'y'wz$	$\bar{x}'y'wz'$	0100	4
$\bar{x}y 11$	$\bar{x}y'wz'$	$\bar{x}y'wz$	$\bar{x}y'wz$	$\bar{x}y'wz'$	0101	5
$\bar{x}y' 10$	$\bar{x}y'wz'$	$\bar{x}y'wz$	$\bar{x}y'wz$	$\bar{x}y'wz'$	0110	6
	0	1	3	2		
	4	5	7	6		
	12	13	15	14		
	8	9	11	10		

maxterms

	$wz$	$wz'$	$w'z'$	$w'z$
	00	01	11	10
$\bar{x}y 00$	$\bar{x}+y+z+w$	$\bar{x}+y+w+z'$	$\bar{x}+y+w'+z'$	$\bar{x}+y+w'+z$
$\bar{x}y' 01$	$\bar{x}+y'+w+z$	$\bar{x}+y'+w+z'$	$\bar{x}+y'+w'+z'$	$\bar{x}+y'+w'+z$
$\bar{x}y' 11$	$\bar{x}'+y'+w+z$	$\bar{x}'+y'+w+z'$	$\bar{x}'+y'+w'+z$	$\bar{x}'+y'+w'+z'$
$\bar{x}y' 10$	$\bar{x}'+y+w+z$	$\bar{x}'+y+w+z'$	$\bar{x}'+y+w'+z$	$\bar{x}'+y+w'+z'$
	0	1	3	2
	4	5	7	6
	12	13	15	14
	8	9	11	10

Q-1 Simplify given boolean function by K map.

$$f(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

$\bar{x}y' 00$	0	1	1	3	$\bar{x}w'$
$\bar{x}y' 01$	4	1	5	7	$\bar{x}$
$\bar{x}y 11$	12	1	13	15	$yw'$
$\bar{x}y' 10$	7	1	9	11	$wz'$

$$F = \bar{z}' + \bar{x}w' + yw'.$$


$$F = A\bar{C} + \bar{B}\bar{D} + \bar{A}D \quad \text{SOP form}$$

$$= (A+B+D) (\bar{A}+\bar{C}+\bar{D}) (\bar{A}+\bar{B}+\bar{C})$$

### \* Implementation


AND, OR, Inverter Logic.

SOP  $\Rightarrow$

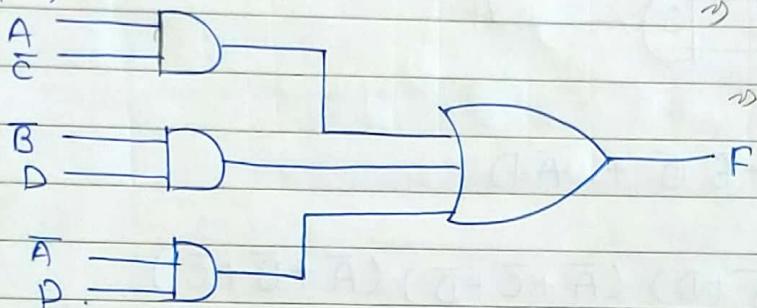

POS  $\Rightarrow$
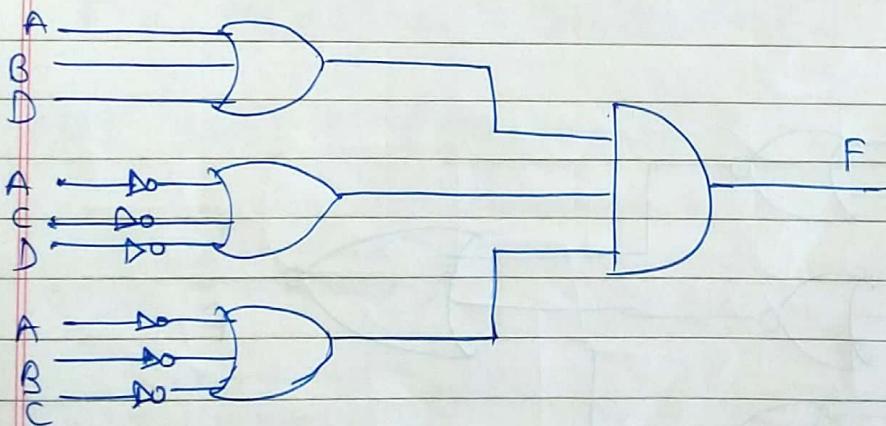
$$f = (A+B+D) (\bar{A}+\bar{C}+\bar{D}) (\bar{A}+\bar{B}+\bar{C})$$




### \* Implementation by using universal logic.

$$f = A\bar{C} + B\bar{D} + \bar{A}D$$

$$f' = \overline{A\bar{C} + B\bar{D} + \bar{A}D}$$

$$(f') = (\overline{A\bar{C}}) \cdot (\overline{B\bar{D}}) \cdot (\overline{\bar{A}D})$$
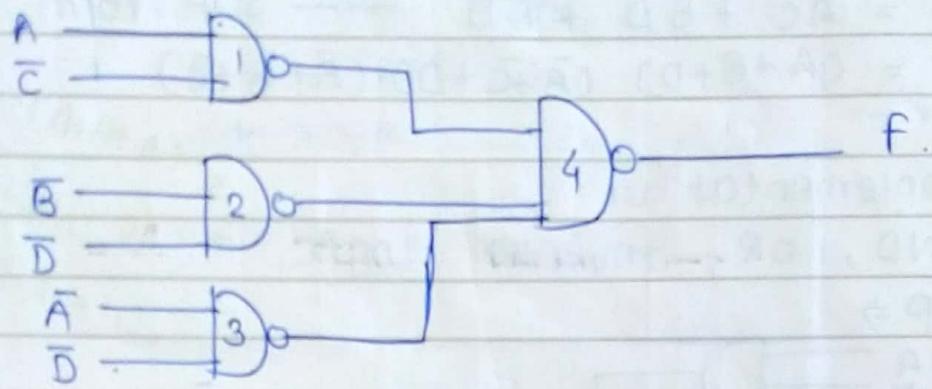
$$(f')' = \overline{(\overline{A\bar{C}}) \cdot (\overline{B\bar{D}}) \cdot (\overline{\bar{A}D})}$$




$$F = AC + BD + \bar{A}D$$

$$= (A + \bar{B} + D)(\bar{A} + \bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C})$$

$$= \overline{(A + \bar{B} + D)} + \overline{(\bar{A} + \bar{C} + \bar{D})} + \overline{(\bar{A} + \bar{B} + \bar{C})}$$

$$= \overline{(A + \bar{B} + D)} + \overline{(\bar{A} + \bar{C} + \bar{D})} + \overline{(\bar{A} + \bar{B} + \bar{C})}$$

=

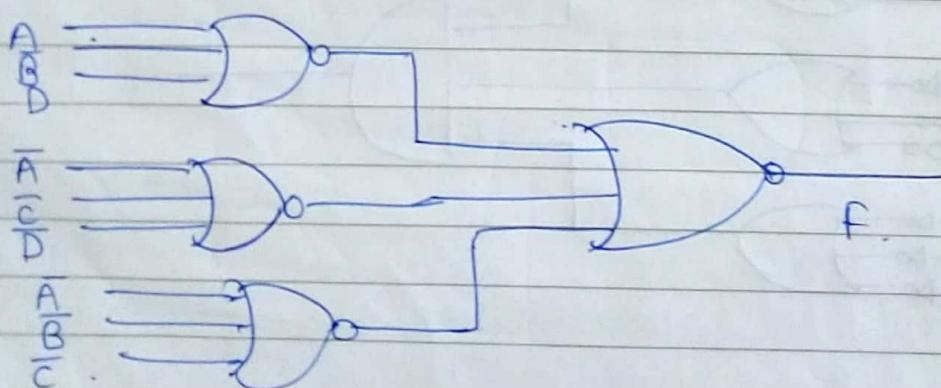

Q. Reduce expression using K-map

$\Pi(2, 8, 9, 10, 11, 12, 14)$  and implement it in AOI logic, NAND, NOR logic.

→

				POS
				$w' + z$
				$w' + z'$
maxterms	$w + z$	$w + z'$	$w' + z'$	$w' + z$
	00	01	11	10
$x + y$	00	0	1	3
$x + y'$	01	4	5	7
$x'y + y'$	11	12	13	15
$x'y$	10	8	9	11
				10
				14
				16
				17
				18
				383

$\Sigma(0, 1, 3, 4, 5, 6, 7, 13, 15)$ ,  $Z'$

$w'z'$	$w'z$	$wz$	$wz'$
00	01	11	10
$x'y'z' = 00$	$x'y'z = 01$	$x'yz = 11$	$xy'z = 10$
$x'y'z' = 00$	$x'y'z = 01$	$x'yz = 11$	$xy'z = 10$
$x'y'z' = 00$	$x'y'z = 01$	$x'yz = 11$	$xy'z = 10$

$$f = yz + x'y + x'w' + x'wz$$


$$f = yz + x'y + x'w' + x'wz$$

$$f' = \overline{yz + x'y + x'w' + x'wz}$$

$$\Rightarrow \overline{yz} \cdot \overline{x'y} \cdot \overline{x'w'} \cdot \overline{x'wz}$$

$$(f')' \Rightarrow \overline{\overline{yz} \cdot \overline{x'y} \cdot \overline{x'w'} \cdot \overline{x'wz}}$$

### \* NAND Implementation

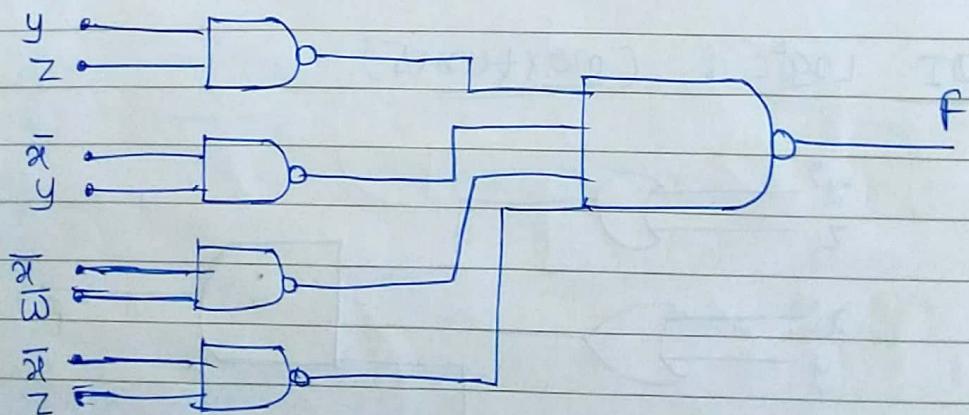


$$f = (x' + z) \cdot (x' + y) \cdot (y + w' + z)$$

$$f' = \overline{(x' + z) \cdot (x' + y) \cdot (y + w' + z)}$$

$$= (x' + z) + (x' + y) + (y + w' + z)$$

$$(f')' \Rightarrow \overline{(x' + z) + (x' + y) + (y + w' + z)}$$

## \* NOR Implementation:

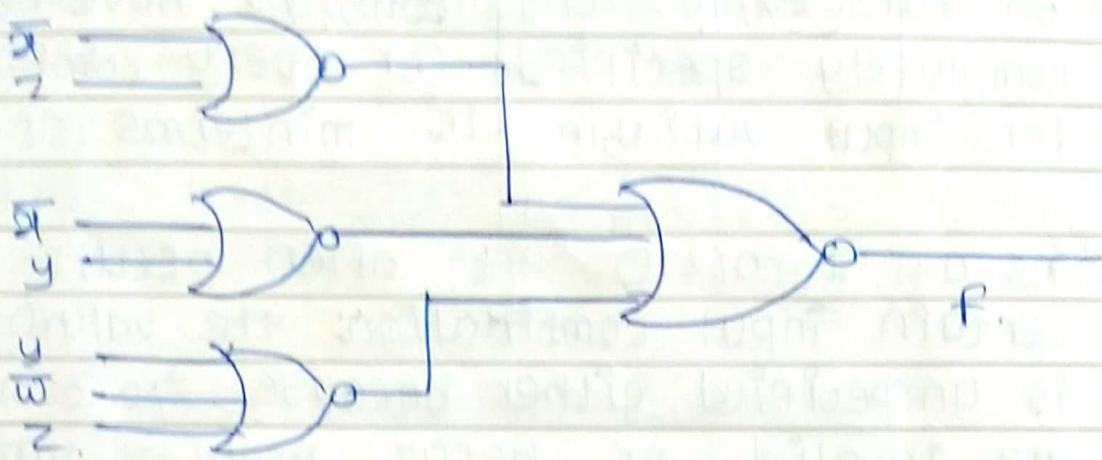

$$A+B+\bar{A}\bar{B}C+\bar{C}\bar{C}$$

$$A+B+c(\bar{A}\bar{B}+\bar{C})$$

$$\bar{A}\bar{A}+\bar{B}\bar{B}+A+B+\bar{A}\bar{B}C$$

$$AB+\bar{A}\bar{B}C+\bar{A}B\bar{A}Q$$

$$(A)(\bar{B})+(\bar{A})(B) = AB + \bar{A}\bar{B}$$

$$AA+BB+\bar{A}\bar{B}C$$

$$(A+B)+(\bar{A}\bar{B}C)$$

$$(A+B+\bar{A}\bar{B}) \cdot (\bar{A}B+C)$$

## \* Don't care combinations

- so far expressions consider have been completely specified for every combinations for input variable ie minterms or maxterms
- As a 1 or 0 it often occurs that for certain input combination the value of output is unspecified either because i/p combinations are invalid or becaz. precise value of o/p is of no consequence.
- The combinations for which values of expression are not specified are called don't care combinations & such expression are therefore stand incompletely specified.
- The o/p is don't care for this invalid combination

eg

in excess-3 code system binary states are unspecified and never occur. These are called don't cares

similarly in 8421 code, binary sets from 10 to 15 are invalid or and corresponding o/p are don't care.

- - Don't care terms are denoted by X or  $\phi$ .
- - During process of design using sop map each don't care is treated as '1' if it is helpful in map reduction otherwise it is treated as zero '0' & left alone.

$$\text{maxterms} = (B+D)(\bar{A}+B)(\bar{C}+\bar{D})$$

$$\text{min} = BC + \bar{B}D + \bar{A}\bar{C}D$$

Date \_\_\_\_\_ / \_\_\_\_\_ / \_\_\_\_\_

Saathai

- During process of design using pos form map each don't care is treated as zero if it is useful in map reduction, otherwise it is treated as 1 & left alone.

Q.1 Reduce expression  $\Sigma_m(1, 5, 6, 12, 13, 14) + \phi(2, 4)$ . and implement it in universal logic.

mpn terms	$C'D'$	$C'D$	$CD$	$CD'$
00	0	1	1	3
$A'B$	4	5	7	6
$AB$	12	13	15	14
10	8	9	11	10


$$f = BC' + D'B + C'DA'$$

$$f' = \overline{BC' + D'B + C'DA'}$$

$$(f')' = \overline{(B\bar{C}) \cdot (\bar{D}B) \cdot (\bar{C}D\bar{A})}$$

$$(f')' = \overline{\bar{B}\bar{C} \cdot \bar{D}B \cdot \bar{C}D\bar{A}}$$

using NAND gates

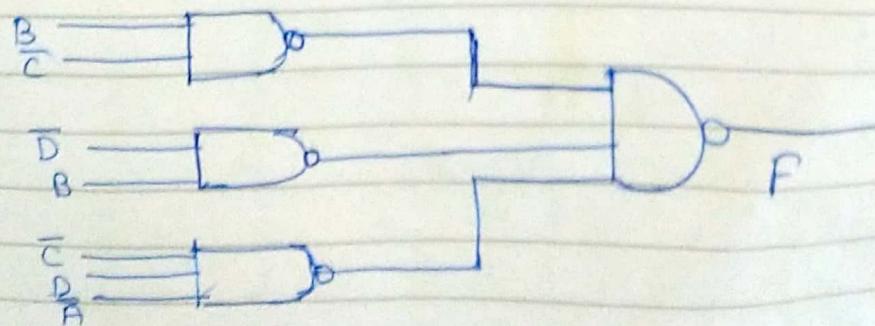

$\Sigma m(3, 4, 7, 9, 10, 11) + d(0, 2, 13, 14, 15)$ 

(Saathi)

Data  
min terms

	$\bar{C}D$	$\bar{C}D$	$CD$	$C\bar{D}$
$A\bar{B}$	X		1	1
$\bar{A}B$	1			
$A B$		X	(X)	X
$A\bar{B}$		1	1	1

$\bar{A}C \leftarrow A\bar{B}$        $AC \rightarrow C\bar{D}$

$\downarrow AD$        $\downarrow CD$

$$f = AD + CD + AC + \bar{A}\bar{C}\bar{D}$$

	$C+D$	$C+D$	$\bar{C}+\bar{D}$	$\bar{C}+D$
$A+B$	X	(X)	(X)	X
$A+\bar{B}$	(X)	0	0	0
$\bar{A}+\bar{B}$	0	X	X	X
$\bar{A}+B$	0	0	0	X

$\bar{B} + \bar{C} + D \rightarrow$

$\bar{A} + C + D \leftarrow \bar{A} + B$

$$T_M = (1, 5, 6, 8, 12) + d(0, 2, 13, 14, 15)$$

H H

K

## Clipper :



clipper - Waveform is shaped by removing some part of input signal is called as clipper.

**TYPES OF CLIPPER CIRCUIT :**


- 1) Positive clipper.
- 2) Negative clipper.
- 3) Combinational clipper.
- 4) Biased clipper
  - Positive biased
  - Negative biased
  - Combinational clipper.
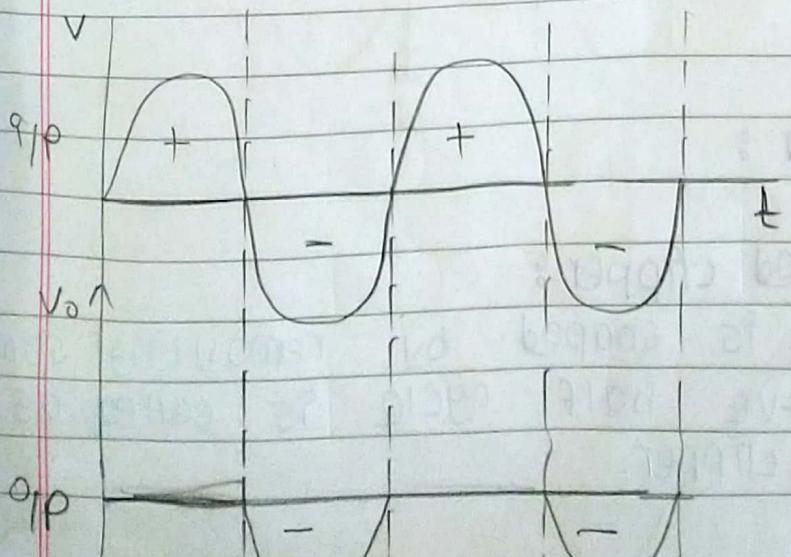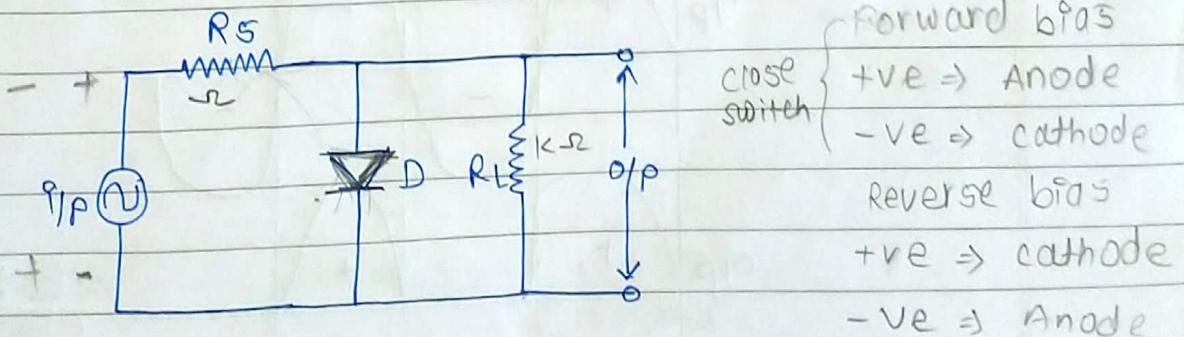
### 1) Positive clipper :

In this circuit positive half cycle is removed.




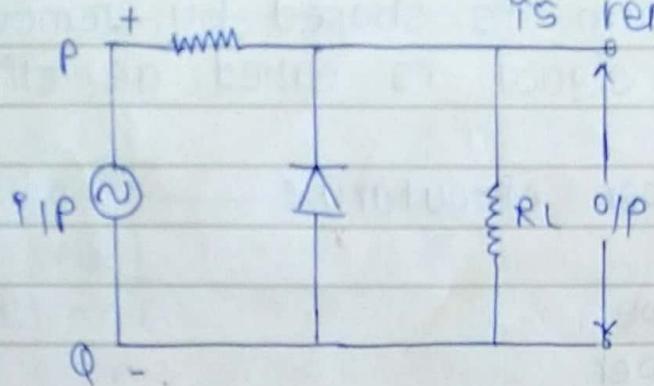\* Negative clipper : In this negative half cycle is removed.




- 1) During +ve half cycle p is +ve and q is -ve so diode is in reverse bias so it acts as reverse open switch.  
so we get o/p at RL during +ve cycle
- 2) During -ve half cycle p is -ve & q is +ve diode is in forward bias so acts as close switch.

Waveform :

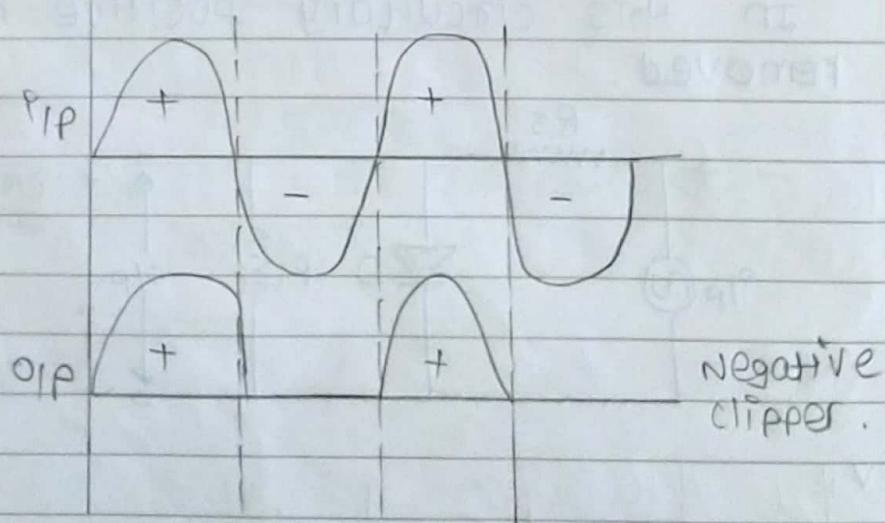

\* Biased clipper :

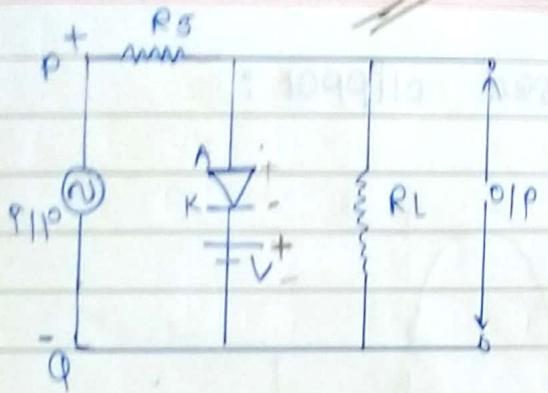
- 1) Positive biased clipper : waveform is shaped by removing some part of +ve half cycle is called as +ve biased clipper.





If battery is  
then it acts  
as positive  
clipper

- during +ve half cycle diode goes in forward bias. but downwards DC voltage reversed the diode in reverse bias upto its voltage  $V$  because +ve terminal of battery connected to cathode of diode.

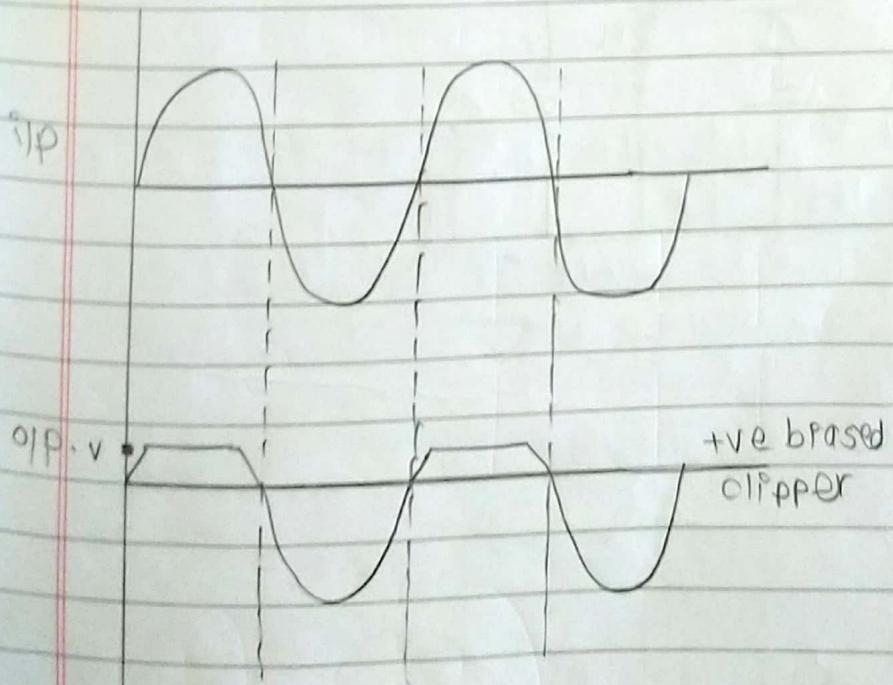*(offset down)*  
After this DC voltage  $V$ , above  $V$  this diode goes in forward bias. so above voltage  $V$  then it acts as closed switch.



Q) Negative biased clipper :

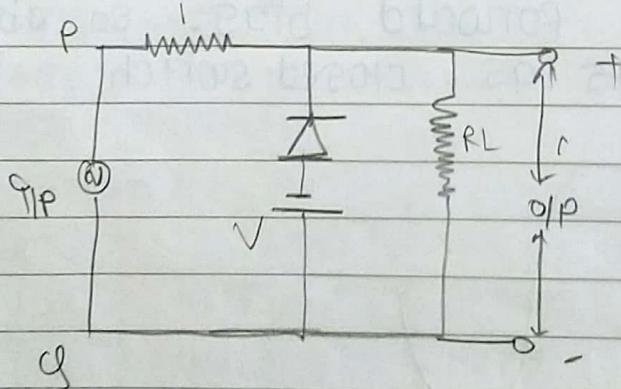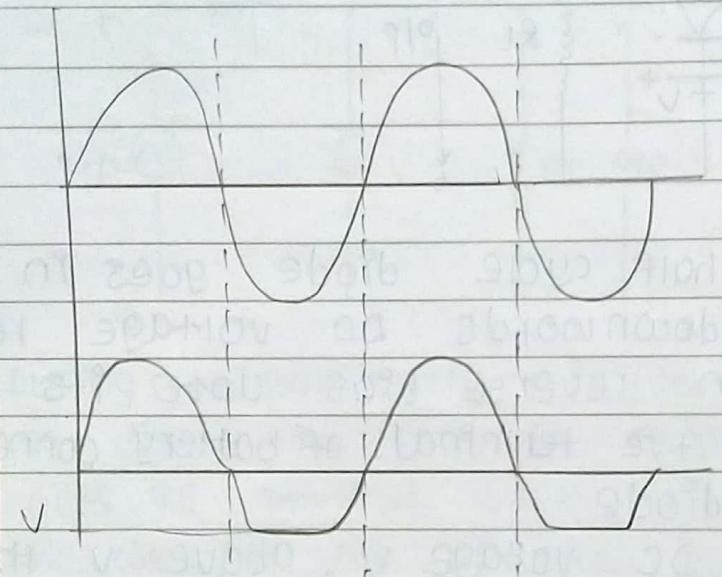

## \* Elamper circuit :

To stamp  $\Rightarrow$  To shift.

## \* Steps of Designing.

- 1) Identify no. of inputs and no. of outputs
- 2) prepare truth table
- 3) obtain boolean expression.
- 4) Reduce expression | boolean function by k-map if necessary
- 5) Implement reduced boolean function or expression by using logic gates according to required logic. (AOI, NAND, NOR).

Q.1 Construct hardware circuit using only NAND gates for

$Y = F(P, Q, R)$  where  $Y$  is true (high 1), if, two or more inputs of  $P | Q | R$  are true (high 1)

→ D 3 inputs & 1 o/p.

Q)

P	Q	R	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

3) obtain boolean function by truth table

$$f = P'Q'R + \cdot P Q' R + P Q R' + P Q R.$$

4) Reduce above function by K-map.

$Q'R'$	$Q'R$	$QR'$	$QR$
00	01	10	11

$P'$	0	0	1	1	1	1	0
$P$	1	1	1	0	0	0	1
$R'$	0	1	0	0	1	1	1
$R$	1	0	1	1	0	0	0

$P'R$        $QR$


NAND logic.

$$f = PR + QR + PQ$$


$$f' = \overline{PR + QR + PQ}$$

$$f'' = \overline{\overline{PR} \cdot \overline{QR} \cdot \overline{PQ}}$$
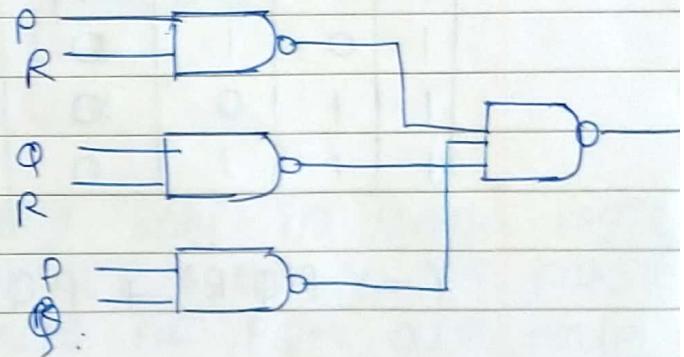
$$f''' = \overline{\overline{PR} \cdot \overline{QR} \cdot \overline{PQ}}$$



AOI logic.

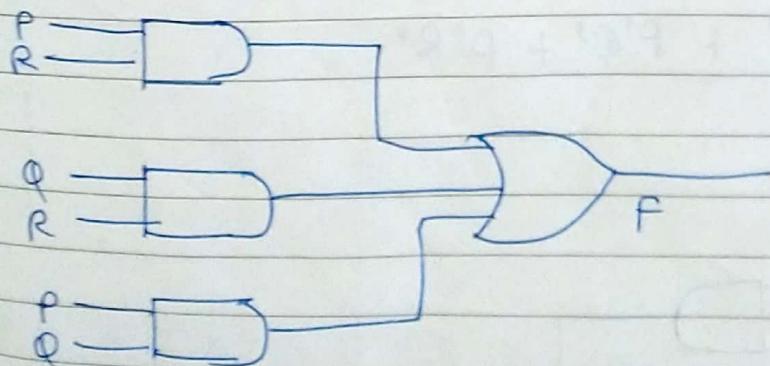

Q.2 construct hardware circuit using NAND logic as well as AOI logic for  $Y = f(P, Q, R)$  where  $Y$  is true if two or more inputs of  $P, Q, R$  are false.

P	Q	R	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


$$Y = P'Q'R' + P'Q'R + P'QR' + PQ'R'$$

			$Q'R'$	$Q'R$	$QR$	$QR'$
$P'$	0	1	1	0	1	1
$P$	1	0	1	0	0	1
			3	2	0	6

$$f = Q'R' + P'Q' + P'R'$$

$$f = Q'R' + P'Q + P'R$$


AOI logic

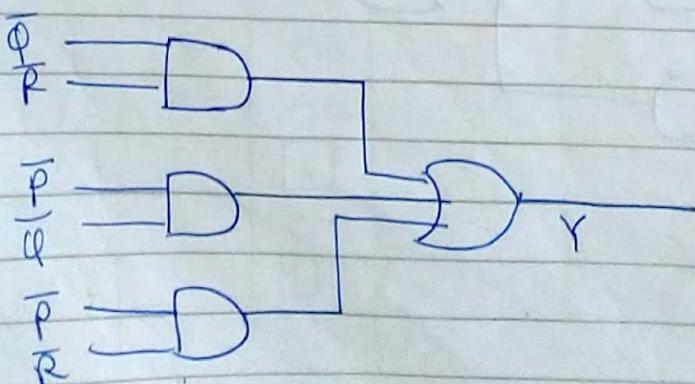

$$f' = \overline{Q'R'} \cdot \overline{P\bar{Q}} \cdot \overline{(PR)}$$

$$f = \overline{\bar{Q}R} \cdot \overline{P\bar{Q}} \cdot \overline{(PR)}$$

NAND Implementation

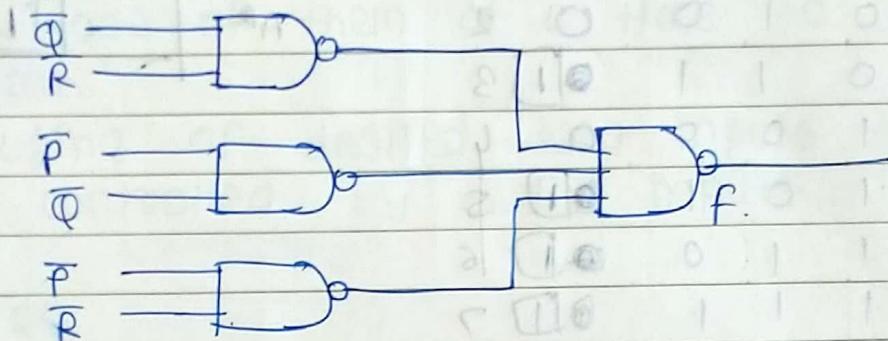

Q.3 construct hardware using only in NAND logic & AOI logic for  $Y = f(P, Q, R)$  Y is false if two or more inputs of PQR are true.

$\rightarrow$	P	Q	R	Y
	0	0	0	1
	0	0	1	1
	0	1	0	1
	0	1	1	0
	1	0	0	1
	1	0	1	0
	1	1	0	0
	1	1	1	0

$$Y = P'Q'R' + P'Q'R + P'QR' + PQR'$$

1	0	1	1	3	1	2
4		5		7	6	

Q.3 CONSTRUCT hardware CKT for NAND & ADD logic  
 $Y(P, Q, R)$   $Y$  is false if two or more inputs  
 of  $P, Q, R$  are false.

P	Q	R	Y
0	0	0	No
0	0	1	0 M
0	1	0	0 2
0	1	1	0 <input checked="" type="checkbox"/> 3
1	0	0	0 4
1	0	1	0 <input checked="" type="checkbox"/> 5
1	1	0	0 <input checked="" type="checkbox"/> 6
1	1	1	0 <input checked="" type="checkbox"/> 7

