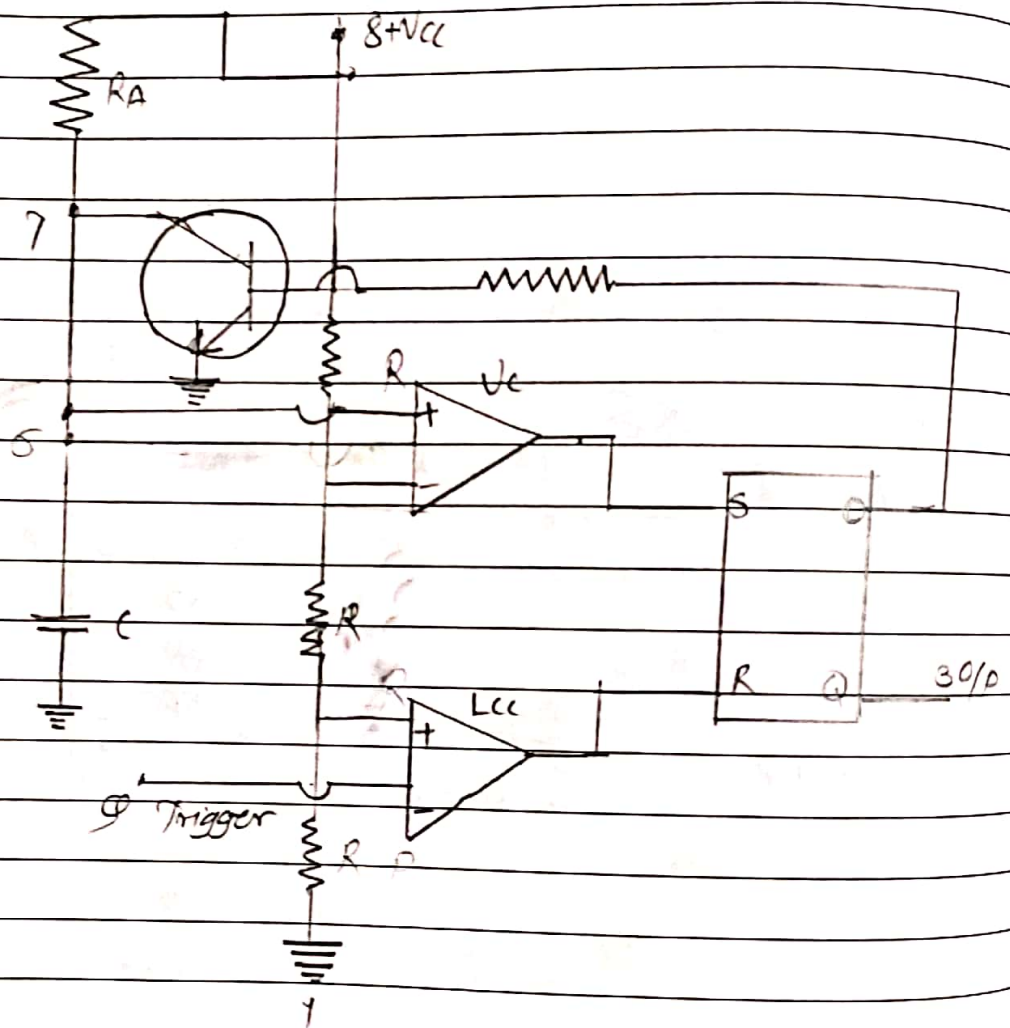



Q3)

Explain working of 555 as a monostable multivibrator with the help of neat circuit diagram. Draw waveform & state the formula for pulse width.



Working :-

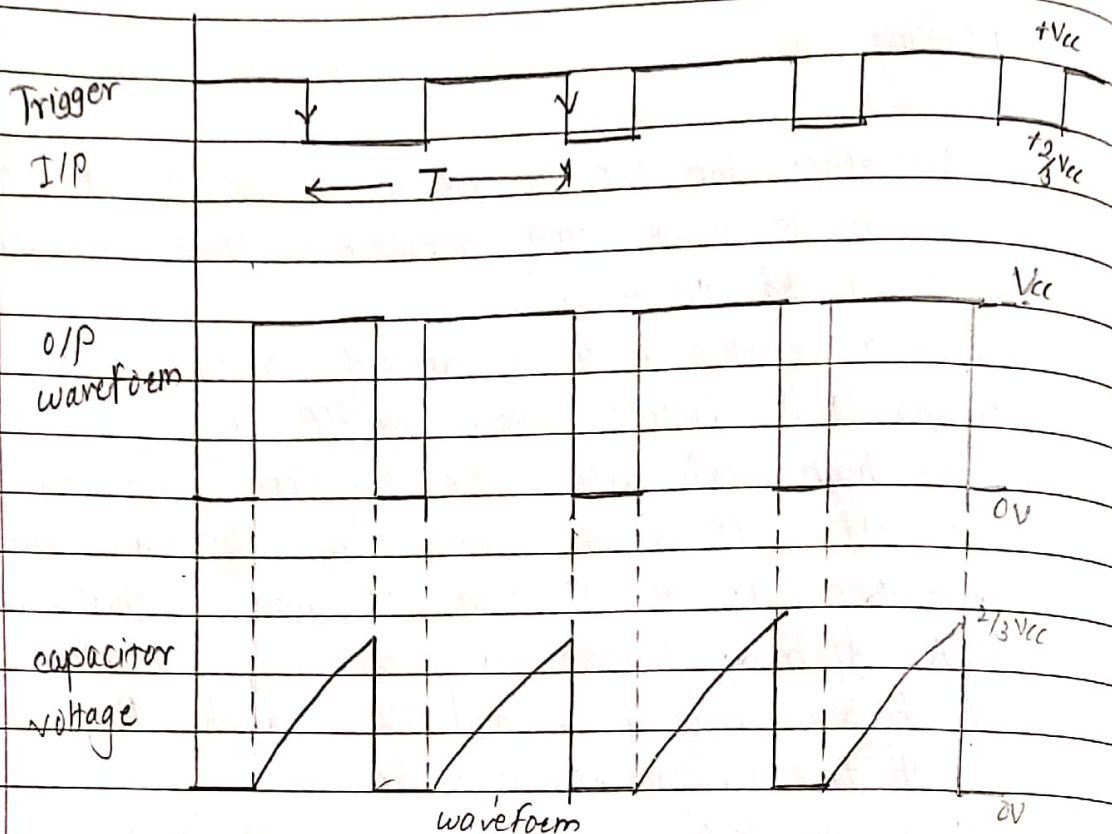- 1) Initially, when O/P at pin 3 is low i.e. circuit is in stable state, the transistor is ON & capacitor C is shorted to ground.
- 2) When a negative pulse is applied to pin 2, the trigger falls below $\frac{1}{3}V_{CC}$. The O/P of comparator goes high which resets the flip-flop & transistor turn off & O/P at pin 3 goes high. This is the transition of the O/P from low to quasi stable state.
- 3) As discharge transistor is cutoff, the capacitor C begins charging toward $+V_{CC}$ through R_1 with time constant equal to R_1C .
- 4) When the increasing capacitor voltage becomes slightly greater than $\frac{2}{3}V_{CC}$, the O/P of comparator 1 goes high which sets the flip-flop. The capacitor C which sets the flip-flop starts discharging & O/P of timer goes low. Thus O/P returns back to stable state from quasi-stable state.
- 5) The O/P of the monostable multivibrator remains low until a trigger pulse is again applied. Then the cycle repeats.



Pulse width $= W = 1.1 RC$.

The voltage across capacitor C at any instant t is given by $V = V_{cc}(1 - e^{-t/RC})$.

T (time constant) is time required for the capacitor to charge from 0 to $\frac{2}{3}V_{cc}$.

$$\therefore V = \frac{2}{3} V_{cc}$$

$$t = T$$

$$\frac{2}{3} V_{cc} = V_{cc} (1 - e^{-t/RC})$$

$$T = RC \log_e \left(\frac{V_{cc}}{V_{cc} - \frac{2}{3}V_{cc}} \right) = 1.1 RC$$

$$\therefore T = 1.1 RC = W = \text{pulse width.}$$