

Assignment 2

PAGE NO. :

DATE : / /

Name:- Pooja Milind Bandgar

PRN:- 2019BTECS00020

class:- FYCSE-2

sub:- Electronics

Q1 Draw the Internal Diagram of IC555

